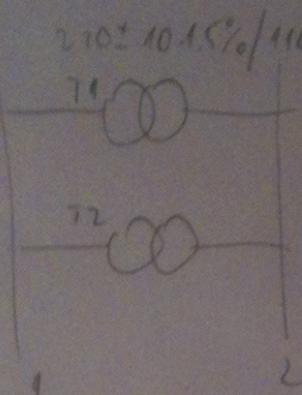


1.



$$270 \pm 10.15\% / 110 \text{ kV}$$

$$S_n = 150 \text{ MVA}$$

$$T_1 : n_1 = 45$$

$$U_e = 10.5 \text{ kV}$$

$$T_2 : n_2 = 0$$

$$P_0 = 0, P_1, P_2 = 0$$

Transf. m u f. norm. fak.

$$U_1 = 231 \text{ kV}$$

$$S_0 = 100 \text{ MVA}$$

$$U_0 = ?$$

$$U_0 - U_n = 110 \text{ kV}$$

$$Y_0 = 0$$

$$Z_r [P_0] = \frac{S_0}{Y_0^2} \cdot \frac{U_n^2}{S_n} \cdot \left[ \frac{P_0}{S_n} + j \sqrt{U_n^2 - \left( \frac{P_0}{S_n} \right)^2} \right] = 0.667 [0 + j 0.105]$$

$$Z_r = j 0.03 \text{ p.u}$$

$$a_{1-T_1} = \frac{270(1+5.0215)}{270} = 1 \quad a_{T_1-T_2} = \frac{270(1+3.0045)}{270} = 1$$

$$Y_T = -14.286 j \text{ p.u}$$

$$d_{2-T_1} = 1 \quad d_{T_2-T_1} = 1$$

$$Y_{12-T_1} : \frac{Y_T}{a_1} = -13.289 j \text{ p.u} \quad d_1 = a_{1-T_1} = 1.075$$


$$Y_{01-T_1} = Y_T \cdot \frac{1}{a_1} \left( \frac{1}{a_1} - 1 \right) = 0.927 j \text{ p.u}$$

$$Y_{12-T_2} = -14.286 j \text{ p.u}$$

$$Y_{01-T_2} = Y_{02-T_2} = 0$$

$$Y_{02-T_1} = Y_T \left( 1 - \frac{1}{a_1} \right) = -0.9967 j \text{ p.u}$$

$$|Y| = \begin{vmatrix} Y_{12-T_1} + Y_{12-T_2} + Y_{01-T_1} & - (Y_{12-T_1} + Y_{12-T_2}) \\ - (Y_{12-T_1} + Y_{12-T_2}) & Y_{12-T_1} + Y_{12-T_2} + Y_{01-T_1} \end{vmatrix}$$

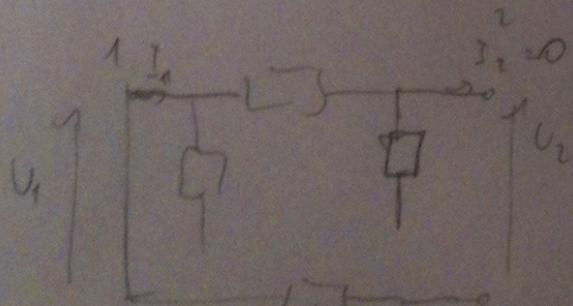

$$|Y| = \begin{vmatrix} -28.4526 j & 28.7606 j \\ 28.7606 j & -18.5718 j \end{vmatrix}$$

$$\begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} -76.648j & 27.578j \\ 27.578j & -28.5917j \end{vmatrix} \begin{vmatrix} U_1 \\ U_2 \end{vmatrix}$$

$$I_1 = Y_{11}U_1 + Y_{12}U_2 \quad U_1 = 231kV$$

$$U_1 = 105p.u$$

$$I_2 = Y_{21}U_1 + Y_{22}U_2 = 0$$

$$U_2 = \frac{-Y_{21}U_1}{Y_{22}} = \frac{-28.5606j}{-28.8918j}$$


~~$$U_2 = 0.8916p.u$$~~

$$U_2 = 1.0134p.u$$

$$U_2 [p.u] = \frac{U_2}{U_{2n}} \Rightarrow U_2 = U_2 [p.u] \cdot 110kV$$

~~$$U_2 = 111.441kV$$~~

2.(1)

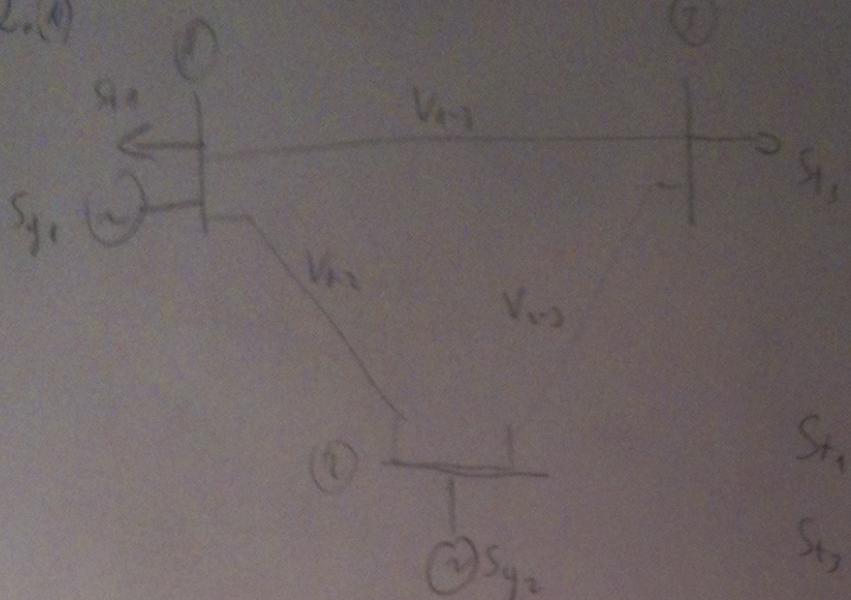

$$|U_1^{(n)}| \angle \frac{\theta_1^{(n)}}{2} = 2$$

$$|U_1^{(n)}| \angle \theta_1^{(n)} = 2$$

$$G \cdot S \cdot Y, d=1$$

$$S_{t1} = 40 + j 10 \text{ MVA}$$

$$S_{t2} = 60 + j 15 \text{ MVA}$$

$$S_{g1} = 50 + j 10 \text{ MVA}$$

$$V_1 = 115 \text{ kV}$$

$$\text{Vodová: } X_1 = 0.42 \Omega / \text{km}$$

$$U_1^{(0)} = U_1^{(n)} - 110 \angle 0^\circ \text{ kV} = 1 \text{ p.u.}$$

$$l = 50 \text{ km}$$

$$S_B = 100 \text{ MVA} \quad U_B = 110 \text{ kV}$$

$$Z_V = j 21 \Omega$$

$$S_1 = 10 \text{ MVA} = 0.1 \text{ p.u.}$$

$$Y_V = -0.04762j \text{ S}$$

$$S_3 = -60 - 15j \text{ MVA} = -0.6 - 0.15j \text{ p.u.}$$

G-S-Y:

$$U_i^{(k+1)} = \frac{K L_i}{U_i^{(k)}} \cdot \sum_{j=1}^{i-1} Y_{Lij} U_j^{(k+1)} - \sum_{j=i+1}^k Y_{Lij} U_j^{(k)} \quad \left. \begin{array}{l} Y_V [\text{p.u.}] = Y_V \cdot \frac{U_B^2}{S_B} \\ = -5.76207j \text{ p.u.} \end{array} \right\}$$

$$K L_i = \frac{S_i}{Y_{ii}}, \quad Y_{Lij} = \frac{Y_{ij}}{Y_{ii}}$$

$$Y = \begin{vmatrix} Y_{v1,1} + Y_{v1,2} & -Y_{v1,2} & -Y_{v1,3} \\ -Y_{v2,1} & Y_{v2,2} + Y_{v2,3} & -Y_{v2,3} \\ -Y_{v3,1} & -Y_{v3,2} & Y_{v3,1} + Y_{v3,2} \end{vmatrix} = \begin{vmatrix} -0.09526j & 0.06362j & 0.04762j \\ 0.05362j & -0.09526j & -0.04762j \\ 0.04762j & 0.05362j & -0.09526j \end{vmatrix}$$

2(2)

$$KL_1 = \frac{S_1}{Y_{11}} = 8.6975 \cdot 10^3 j + 0.0086795 j$$

$$U_2 = \frac{45}{40} + 1.3333 j$$

$$KL_3 = \frac{S_3}{Y_{33}} = -0.013 - 0.0524 j$$

$$Y\{\rho(j)\} = \begin{vmatrix} -11.577704j & 5.76707j & 5.76707j \\ 5.76707j & -11.577704j & 5.76707j \\ 5.76707j & 5.76707j & -11.577704j \end{vmatrix} [\rho(j)]$$

$$YL_{12} = \frac{Y_{12}}{Y_{11}} = YL_{13} = YL_{21} = YL_{23} = YL_{31} = YL_{32} = -0.5$$

$$U_1^{(1)} = \frac{KL_1}{U_1^{(0)*}} - YL_{12} U_2 - YL_{13} U_3^{(0)} = 1.0277 + 0.0086795j$$


$$U_3^{(1)} = \frac{KL_3}{U_3^{(0)*}} - YL_{32} U_2 - Y_{31} U_1^{(1)} = 1.021075 - 0.04476j$$

$$U_1^{(2)} = \frac{KL_1}{U_1^{(1)*}} - YL_{12} U_2 - YL_{13} U_3^{(1)} = 1.03314 - 0.0154j = 1.0333 \angle -0.8579^\circ = 113663 \angle -0.8579^\circ$$


$$U_3^{(2)} = \frac{KL_3}{U_3^{(1)*}} - Y_{32} U_2 - Y_{31} U_1^{(2)} = 1.02587 \angle -32.42^\circ = 112.8454 \angle -32.42^\circ$$

3.

$R[n]$	$X[n]$	$B[nS]$
V1	4	21
V2	4	21

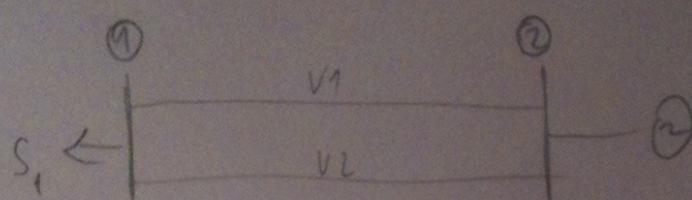

(1)

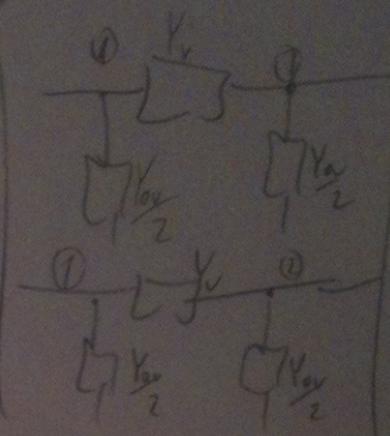

$$U_0 = 110kV$$

$$S_0 = 100MVA$$

$$U_1^{(0)} = 110/0^\circ kV$$

$$U_2 = 110kV = 1 \text{ p.u}$$

$$S_1 = -50 - j15MVA = -0.5 - 0.15j \text{ p.u}$$

$$G = 5, Z = 2, U_1 = ? \text{ u2 } \epsilon = 10^{-2}.$$

$$Z_v = 4 + j21 \Omega \approx$$

$$Y_{ov} = j0.000145$$

$$Z_v[\text{p.u}] = Z_v \cdot \frac{S_0}{U_0^2} = 0.03306 + 0.17355j \text{ p.u} \quad Y_{av}[\text{p.u}] = Y_{ov} \cdot \frac{U_1^2}{S_0} = 0.01694j \text{ p.u}$$

$$Y_{v1} = Y_{v2} = 1.0581 - 5.5602j \text{ p.u}$$

$$\frac{Y_{ov}}{2} = 0.00847j \text{ p.u}$$

$$Y = \begin{vmatrix} Y_v + Y_v & -(Y_v + Y_v) \\ -(Y_v + Y_v) & Y_v + Y_v \end{vmatrix} = \begin{vmatrix} 2.1182 - 11.1204j & -2.1182 + 11.1204j \\ -2.1182 + 11.1204j & 2.1182 - 11.1204j \end{vmatrix}$$

$$Y' = \begin{vmatrix} \frac{Y_{ov} + Y_{ov}}{2} & \frac{Y_{ov} - Y_{ov}}{2} \\ \frac{Y_{ov} - Y_{ov}}{2} & \frac{Y_{ov} + Y_{ov}}{2} \end{vmatrix} = \begin{vmatrix} Y_{sv} \\ Y_{vv} \end{vmatrix} = \begin{vmatrix} 0.01694j \\ 0.01694j \end{vmatrix}$$

$\Im(2)$

$Y_2$

$$Y_{11} = 7.1182 - 111206j$$

$$Z_{11} = 0.01653 + 0.08677j$$

$$Y_1 = 0.01644j$$

$$I_1^{(0)} = \frac{S_1^x}{U_1^{x(0)}} - U_1^{(0)} \cdot Y_1' = -0.5 + 0.13306j$$

$$U_1^{(1)} = U_2 + Z_{11} I_1^{(0)} = 0.98019 - 0.011185j \text{ p.v.} \quad |U_1^{(1)} - U_1^{(0)}| = 0.0459 > \epsilon$$

$$I_1^{(1)} = \frac{S_1^x}{U_1^{x(1)}} - U_1^{(1)} Y_1' = -0.50348 + 0.15055j$$

$$U_1^{(2)} = U_2 + Z_{11} I_1^{(1)} = 0.99887 \angle -2.4054^\circ \quad |U_1^{(2)} - U_1^{(1)}| = 2.18585 \cdot 10^{-3} < \epsilon \text{ v.v.}$$

$$= 0.998 - 0.0411j$$

$$U_1^{(2)} = 109.6959 \angle -2.4054^\circ \cancel{\text{ bV}}$$

4. (1)

$$U_1 = 10.5 \angle 0^\circ \text{ kV} = 1 \text{ p.u}$$

$$U_2 = 106.03 \angle -4.07^\circ \text{ kV} = 0.9639 - 0.0684 \text{ j p.u} = 0.9639 \angle -4.07^\circ$$

$$U_3 = 100.36 \angle -9.50^\circ \text{ kV} = 0.901 - 0.1491 \text{ j p.u} = 0.9133 \angle -9.40^\circ$$

~~$$P_g = P_i = 1 \left[ 0.9639 \cdot 12.9055 \cdot \cos(0 + 4.07 - 176.55) \right] = 0.5383 \text{ p.u} = 538.3 \text{ MW}$$~~

~~$$P_t = P_3 = 0.9133$$~~

~~$$12.9055 \angle 176.55^\circ \quad 12.9055 \angle 96.55^\circ \quad 0$$~~

~~$$\gamma = 12.9055 \angle 86.55^\circ$$~~

~~$$-86.363$$~~

$$Y = \begin{vmatrix} Y_T & -Y_T & 0 \\ -Y_T & Y_T + Y_V & -Y_V \\ 0 & -Y_V & Y_V \end{vmatrix} = \begin{vmatrix} 7.2727 \angle 293.25^\circ & 7.2727 \angle 43.25^\circ & 0 \\ 12.9055 \angle 176.55^\circ & 12.9055 \angle 96.55^\circ & 0 \\ 5.66 \angle 100.91^\circ & 5.66 \angle 30.91^\circ & 0 \end{vmatrix}$$

~~$$P_{13} = 1 \cdot 0.9639 \cdot 7.2727 \cdot \cos(0 + 4.07 - 176.55) = +0.0554 \text{ p.u} =$$~~

~~$$P_2 = 0.9639 \left[ 1 \cdot 7.2727 \cdot \cos(-4.07 - 0 - 93.25^\circ) + 0.9133 \cdot 5.66 \cdot \cos(-4.07 + 44 - 100.91^\circ) \right]$$

$$= -0.8697640 \cdot 0.9639 \cdot (-0.8295 - 0.4409) = -1.1692 \text{ p.u}$$~~

4.(2)

$$P_2 = P_1 = 1 \cdot [1 \cdot 7.2727 \cdot \cos(-273.257) + 0.9639 \cdot 7.2727 \cdot \cos(4.07 - 93.257)] \\ = 0.51266 \text{ p.u}$$

$$P_2 = 0.9639 \cdot [1 \cdot 7.2727 \cdot \cos(-4.07 - 93.257) + 0.9639 \cdot 12.9055 \cdot \cos(-736.557) \\ + 0.9133 \cdot 5.66 \cdot \cos(-4.07 + 9.4 - 100.78)] \\ = 0.9639 \cdot [-0.3295 + 1.418988 - 0.4909] \\ = 5.071 \cdot 10^{-4} \text{ p.u} \quad 5.0541 \cdot 10^{-4} \text{ p.u}$$

$$P_t = P_3 = 0.9133 \cdot [0.9639 \cdot 5.66 \cdot \cos(-9.4 - 4.07 - 100.78) \\ + 0.9133 \cdot 5.66 \cdot 0.005(-280.78)] \\ = -0.48437 \text{ p.u}$$

$$P_g = 51.266 \text{ MW}$$

$$P_t = -49.959 \text{ MW}$$

$$P_{bus} = \sum_i P_i = 0.01359 \text{ p.u} \\ = 1.36 \text{ MW}$$

$$S_{\text{v}}) P_{\text{bus}} [\text{MW}] = ?$$

T

$$S_n = 80 \text{ MVA}$$

$$\mu_t = 11.0\%$$

$$P_k = 0.5 \text{ MW}$$

$$U_{n1}/U_{n2} = 105/110 \text{ V}$$

V

$$U_n = 110 \text{ kV}$$

$$R_n = 0.08 \Omega/\text{km}$$

$$X_n = 0.12 \Omega/\text{km}$$

$$B_n = 0 \mu\text{s/km}$$

$$l = 50 \text{ km}$$

$$U_0 = 105 \text{ V}$$



$$S_0 = 900 \text{ MVA}$$

$$P_0 = 0 \text{ MW}$$

$$f_n = f_m = \omega$$

$$U_1 = 11.0 \angle 0^\circ \text{ kV}$$
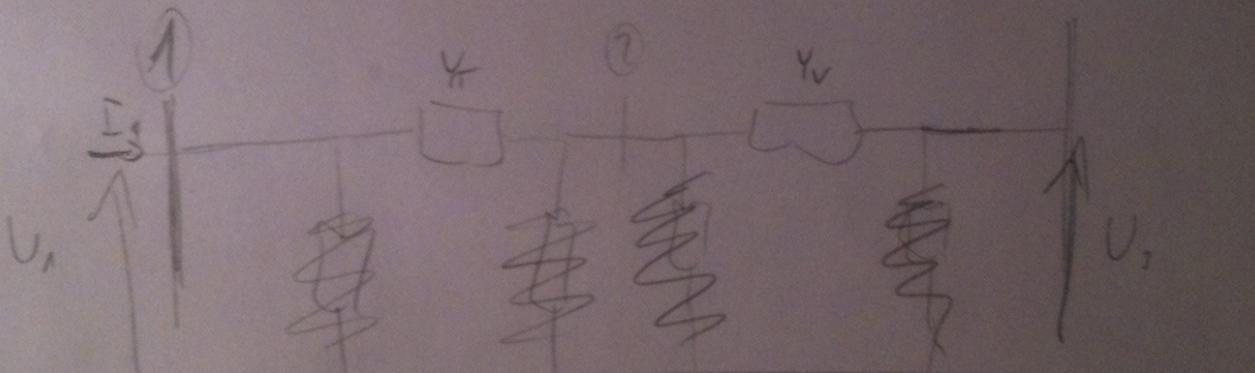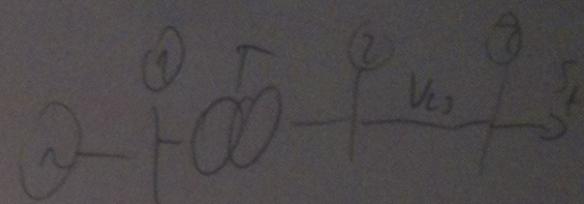
$$U_2 = 110.05 \angle -4.88^\circ \text{ kV}$$



$$Z_T = \frac{S_0}{Y_0^2} \cdot \frac{U_0^2}{S_n} \left[ \frac{P_0}{S_n} + j \sqrt{Y_0^2 - \left( \frac{P_0}{S_n} \right)^2} \right] \Rightarrow Y_T = 0.4132 - 9.76048j \text{ p.u}$$

$$a_1 = a_2 = 1$$

$$Y_{n1} = Y_T$$

$$Y_0 = 0$$


$$Z_V = (0.08 + j0.42) \cdot 50 = 4 + j21 \Omega$$

$$Y_V = 8.25 \cdot 10^{-3} - j0.0459 \text{ S}$$

$$V_V[\text{p.u}] = Y_V \cdot \frac{U_0^2}{S_n} = 10531 - 55602j \text{ p.u}$$

$$Y_{n2} = 0$$

5.

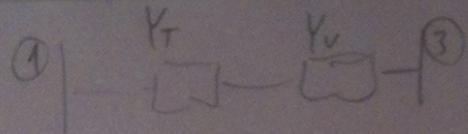

$$Y = \begin{vmatrix} 12.9055 \angle 276.55^\circ & 12.9055 \angle 96.551^\circ \\ 12.9055 \angle 96.551^\circ & 12.9055 \angle 276.55^\circ \end{vmatrix} \quad U_1 = 1.04762 \angle 0^\circ \\ U_2 = 1.00045 \angle -4.88^\circ$$

$$P_1 = 1.04762 \cdot [1.04762 \cdot 12.9055 \cdot \cos(-276.55^\circ) + 1.00045 \cdot 12.9055 \cdot \cos(4.88 - 96.551)] \\ = 1.22115 \text{ p.u}$$

$$P_2 = 1.00045 \cdot [1.04762 \cdot 12.9055 \cdot \cos(-4.88 - 96.551) + 1.00045 \cdot 12.9055 \cdot \cos(-276.55)] \\ = -1.20715 \text{ p.u}$$

$$P_{gas} = \xi P_i = 0.01395 \text{ p.u}$$

$$P_{gas} = 1.4 \text{ MW}$$